

ECS 409: Computer Organization – Assignment 2

Adheesh Trivedi

2025-09-10

Problem 1: Multiply 4-bit by 2

Behavioral code multiplies input by 2 using shift.

```
module MULTBY2(input [3:0] I, output [3:0] O, output carry);

    assign O = I << 1;
    assign carry = I[3];

endmodule

`timescale 1ns / 1ps

module TEST();
    reg [3:0] I;
    wire [3:0] O;
    wire carry;

    MULTBY2 M(I, O, carry);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q1.vcd");
        $dumpvars(0, TEST);

        $display("");
        $display("I      O      Carry");
        $display("-----");
        $monitor("%b %b %b", I, O, carry);

        I = 4'b0000; #10;
        I = 4'b0001; #10;
        I = 4'b0010; #10;
        I = 4'b0111; #10;
        I = 4'b0100; #10;
        I = 4'b1010; #10;
        I = 4'b1111; #10;

        end
    endmodule
```

4-bit x2 multiplier



→ vvp q1.vvp

Solution by Adheesh Trivedi

=====

VCD info: dumpfile q1.vcd opened for output.

I 0 Carry

0000 0000 0

0001 0010 0


0010 0100 0

0111 1110 0

0100 1000 0

1010 0100 1

1111 1110 1

 

Problem 2: 4-to-2 Encoder & 2-to-4 Decoder

Encoder and decoder implemented behaviorally.

```

module ENC4T02(
    input [3:0] I,
    output reg [1:0] O
);
    always @(I) begin
        case (I)
            4'b0001: begin O = 2'b00; end
            4'b0010: begin O = 2'b01; end
            4'b0100: begin O = 2'b10; end
            4'b1000: begin O = 2'b11; end

            endcase
        end
    endmodule

`timescale 1ns / 1ps

module TEST();
    reg [3:0] I;
    wire [1:0] O;

    ENC4T02 E(I, O);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q2_enc.vcd");
        $dumpvars(0, TEST);

        $display("I      O");
        $display("-----");
        $monitor("%b %b", I, O);

        I = 4'b0001; #10;
        I = 4'b0010; #10;
        I = 4'b0100; #10;
        I = 4'b1000; #10;

        end
    endmodule

```

4-to-2 Encoder

```

module DEC2T04(
    input [1:0] I,
    output reg [3:0] O
);
    always @(I) begin
        case (I)
            2'b00: begin O = 4'b0001; end
            2'b01: begin O = 4'b0010; end
            2'b10: begin O = 4'b0100; end
            2'b11: begin O = 4'b1000; end

            endcase
        end
    endmodule

`timescale 1ns / 1ps

module TEST();
    reg [1:0] I;
    wire [3:0] O;

    DEC2T04 D(I, O);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q2_dec.vcd");
        $dumpvars(0, TEST);



        $display("I  O");
        $display("-----");
        $monitor("%b %b", I, O);

        I = 2'b00; #10;
        I = 2'b01; #10;
        I = 2'b10; #10;
        I = 2'b11; #10;

        end
    endmodule

```

2-to-4 Decoder

  



```
→ vvp q2_enc.vvp
Solution by Adheesh Trivedi
=====
VCD info: dumpfile q2_enc.vcd opened for output.
I    0
-----
0001 00
0010 01
0100 10
1000 11
```



```
→ vvp q2_dec.vvp
Solution by Adheesh Trivedi
=====
VCD info: dumpfile q2_dec.vcd opened for output.
I    0
-----
00 0001
01 0010
10 0100
11 1000
```

Problem 3: 8-to-1 Multiplexer

Case statement selects one of 8 inputs.

```

module MUX8T01(
    input [7:0] I,
    input [2:0] S,
    output reg O
);
    always @(I, S) begin
        case (S)
            3'b000: O = I[0];
            3'b001: O = I[1];
            3'b010: O = I[2];
            3'b011: O = I[3];
            3'b100: O = I[4];
            3'b101: O = I[5];
            3'b110: O = I[6];
            3'b111: O = I[7];
            default: O = 1'b0;

            endcase
        end
    endmodule

`timescale 1ns / 1ps

module TEST();
    reg [7:0] I;
    reg [2:0] S;
    wire O;

    MUX8T01 M(I, S, O);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q3.vcd");
        $dumpvars(0, TEST);

        $display("I      S      O");
        $display("-----");
        $monitor("%b %b %b", I, S, O);

        I = 8'b00000000; S = 3'b000; #10;
        I = 8'b00000001; S = 3'b000; #10;
        I = 8'b00000010; S = 3'b001; #10;
        I = 8'b00000100; S = 3'b010; #10;
        I = 8'b00001000; S = 3'b011; #10;
        I = 8'b00010000; S = 3'b100; #10;
        I = 8'b00100000; S = 3'b101; #10;
        I = 8'b01000000; S = 3'b110; #10;
        I = 8'b10000000; S = 3'b111; #10;
        I = 8'b11111111; S = 3'b111; #10;
        I = 8'b10101010; S = 3'b101; #10;
        I = 8'b01010101; S = 3'b010; #10;


        end
    endmodule

```

```

→ vvp q3.vvp
Solution by Adheesh Trivedi
=====
VCD info: dumpfile q3.vcd opened for output.
I      S  O
-----
00000000 000 0
00000001 000 1
00000010 001 1
00000100 010 1
00001000 011 1
00010000 100 1
00100000 101 1
01000000 110 1
10000000 111 1
11111111 111 1
10101010 101 1
01010101 010 1

```

 

Problem 4: 8-to-3 Priority Encoder

If-else logic encodes highest active input.

```

module PRIOENC8T03(
    input [7:0] I,
    output reg [2:0] O,
    output reg valid
);
    always @(I) begin
        if (I[7]) begin O = 3'b111; end
        else if (I[6]) begin O = 3'b110; valid = 1; end
        else if (I[5]) begin O = 3'b101; valid = 1; end
        else if (I[4]) begin O = 3'b100; valid = 1; end
        else if (I[3]) begin O = 3'b011; valid = 1; end
        else if (I[2]) begin O = 3'b010; valid = 1; end
        else if (I[1]) begin O = 3'b001; valid = 1; end
        else if (I[0]) begin O = 3'b000; valid = 1; end
        else begin O = 3'b000; valid = 0; end
    end
endmodule

`timescale 1ns / 1ps

module TEST();
    reg [7:0] I;
    wire [2:0] O;
    wire valid;

    PRIOENC8T03 P(I, O, valid);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q4.vcd");
        $dumpvars(0, TEST);

        $display("I          O Valid");
        $display("-----");
        $monitor("%b %b %b", I, O, valid);

        I = 8'b00000000; #10;
        I = 8'b00000001; #10;
        I = 8'b00000010; #10;
        I = 8'b00000100; #10;
        I = 8'b00001000; #10;
        I = 8'b00010000; #10;
        I = 8'b00100000; #10;
        I = 8'b01000000; #10;
        I = 8'b10000000; #10;
        I = 8'b11111111; #10;
        I = 8'b10101010; #10;
        I = 8'b01010101; #10;

        end
    endmodule


```

8-to-3 Priority Encoder


```

→ vvp q4.vvp
Solution by Adheesh Trivedi
=====
VCD info: dumpfile q4.vcd opened for output.
I          0 Valid
-----
00000000 000 0
00000001 000 1
00000010 001 1
00000100 010 1
00001000 011 1
00010000 100 1
00100000 101 1
01000000 110 1
10000000 111 1
11111111 111 1
10101010 111 1
01010101 110 1

```

 

Problem 5: 4-bit Carry Look-Ahead Adder

Adder uses carry look-ahead logic for fast sum.

```

module CARRY_LOOKAHEAD4 (
    input [3:0] A,
    input [3:0] B,
    input Ci,
    output reg [3:0] S,
    output reg Co
);
    reg [3:0] P, G;
    reg [3:0] C;
    integer i;

    always @(*) begin
        G = A & B;
        P = A ^ B;
        C[0] = Ci;

        // Ci+1 = Gi | Pi & Ci
        for (i = 0; i < 3; i++) begin
            C[i+1] = G[i] | (P[i] * C[i]);
        end
        Co = G[3] | (P[3] * C[3]);
        S = P ^ C;

    end
endmodule

`timescale 1ns / 1ps

module TEST();
    reg [3:0] A, B;
    reg Ci;
    wire [3:0] S;
    wire Co;

    CARRY_LOOKAHEAD4 CLA(A, B, Ci, S, Co);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q5.vcd");
        $dumpvars(0, TEST);

        $display("A    B    Ci | S    Co");
        $display("-----");
        $monitor("%b %b %b | %b %b", A, B, Ci, S, Co);

        A = 4'b0000; B = 4'b0000; Ci = 0; #10;
        A = 4'b0001; B = 4'b0001; Ci = 0; #10;
        A = 4'b0010; B = 4'b0011; Ci = 0; #10;
        A = 4'b0100; B = 4'b0101; Ci = 0; #10;
        A = 4'b1010; B = 4'b1001; Ci = 0; #10;
        A = 4'b1111; B = 4'b1111; Ci = 0; #10;

        A = 4'b0000; B = 4'b0000; Ci = 1; #10;
        A = 4'b0001; B = 4'b0001; Ci = 1; #10;
        A = 4'b0010; B = 4'b0011; Ci = 1; #10;
    end
endmodule

```

```

A = 4'b0100; B = 4'b0101; Ci = 1; #10;
A = 4'b1010; B = 4'b1001; Ci = 1; #10;
A = 4'b1111; B = 4'b1111; Ci = 1; #10;

```

```

end
endmodule


```

Carry Look-Ahead Adder

```

→ vvp q5.vvp
Solution by Adheesh Trivedi
=====
VCD info: dumpfile q5.vcd opened for output.
A      B      Ci | S      Co
-----
0000 0000 0 | 0000 0
0001 0001 0 | 0010 0
0010 0011 0 | 0101 0
0100 0101 0 | 1001 0
1010 1001 0 | 0011 1
1111 1111 0 | 1110 1
0000 0000 1 | 0001 0
0001 0001 1 | 0011 0
0010 0011 1 | 0110 0
0100 0101 1 | 1010 0
1010 1001 1 | 0100 1
1111 1111 1 | 1111 1

```

 

Problem 6: 4-bit Wallace Tree Multiplier

Wallace tree structure for fast multiplication.

```

module HALF_ADDER (
    input A,
    input B,
    output S,
    output C
);
    assign S = A ^ B;
    assign C = A & B;

endmodule

module FULL_ADDER (
    input A,
    input B,
    input Ci,
    output S,
    output Co
);
    assign S = A ^ B ^ Ci;
    assign Co = A & B | ((A | B) & Ci);

endmodule

module WALLACE_TREE_MULT4 (
    input [3:0] A,
    input [3:0] B,
    output [7:0] M
);

    // Partial products
    wire [3:0] P0, P1, P2, P3;

    // Generate partial products
    assign P0 = A & {4{B[0]}};
    assign P1 = A & {4{B[1]}};
    assign P2 = A & {4{B[2]}};
    assign P3 = A & {4{B[3]}};

    // Intermediate wires for carries and sums
    wire c1, c2, c3, c4, c5, c6, c7, c8, c9, c10, c11; // added c11
    wire s1, s2, s3, s4, s5, s6; // removed unused s7,s8,s9

    // First bit (no addition needed)
    assign M[0] = P0[0];

    // Second bit
    HALF_ADDER ha1 (P0[1], P1[0], M[1], c1);

    // Third bit - first level
    FULL_ADDER fa1 (P0[2], P1[1], P2[0], s1, c2);
    HALF_ADDER ha2 (s1, c1, M[2], c3);

    // Fourth bit - first level
    FULL_ADDER fa2 (P0[3], P1[2], P2[1], s2, c4);
    FULL_ADDER fa3 (s2, c2, P3[0], s3, c5);
    HALF_ADDER ha3 (s3, c3, M[3], c6);

```

```

// Fifth bit - first level
FULL_ADDER fa4 (P1[3], P2[2], P3[1], s4, c7);
FULL_ADDER fa5 (s4, c4, c5, s5, c8);
HALF_ADDER ha4 (s5, c6, M[4], c9);

// Sixth bit
FULL_ADDER fa6 (P2[3], P3[2], c7, s6, c10);
FULL_ADDER fa7 (s6, c8, c9, M[5], c11);

// Seventh bit
FULL_ADDER fa8 (P3[3], c10, c11, M[6], M[7]);

endmodule

`timescale 1ns / 1ps

module TEST();
  reg [3:0] A, B;
  wire [7:0] M;

  WALLACE_TREE_MULT4 WTM(A, B, M);

  initial begin
    $display("Solution by Adheesh Trivedi");
    $display("=====");
    $dumpfile("q6.vcd");
    $dumpvars(0, TEST);


    $display("A  B  | M");
    $display("-----");
    $monitor("%d %d | %d", A, B, M);

    A = 4'b0000; B = 4'b0000; #10;
    A = 4'b0100; B = 4'b0101; #10;
    A = 4'b1010; B = 4'b1001; #10;
    A = 4'b1111; B = 4'b1111; #10;
    A = 4'b0001; B = 4'b0001; #10;
    A = 4'b0010; B = 4'b0011; #10;
    A = 4'b0110; B = 4'b0011; #10;
    A = 4'b1001; B = 4'b1110; #10;

    end
endmodule

```

Wallace Tree Multiplier

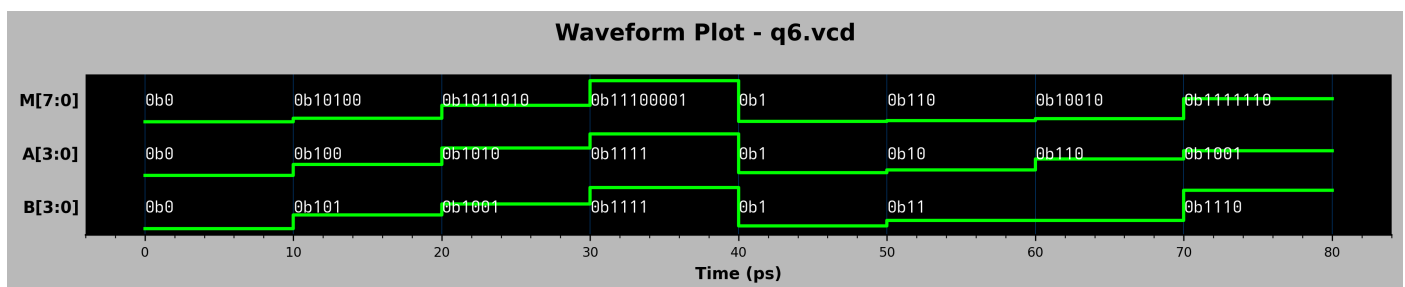



→ vvp q6.vvp

Solution by Adheesh Trivedi

=====

VCD info: dumpfile q6.vcd opened for output.

A B | M

0	0		0
4	5		20
10	9		90
15	15		225
1	1		1
2	3		6
6	3		18
9	14		126