

ECS 409: Computer Organization – Assignment 2

Adheesh Trivedi

2025-09-10

Problem 1: Multiply 4-bit by 2

Behavioral code multiplies input by 2 using shift.

```
module MULTBY2(input [3:0] I, output [3:0] O, output carry);

    assign O = I << 1;
    assign carry = I[3];

endmodule

`timescale 1ns / 1ps

module TEST();
    reg [3:0] I;
    wire [3:0] O;
    wire carry;

    MULTBY2 M(I, O, carry);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $dumpfile("q1.vcd");
        $dumpvars(0, TEST);

        $display("");
        $display("I      O      Carry");
        $display("-----");
        $monitor("%b %b %b", I, O, carry);

        I = 4'b0000; #10;
        I = 4'b0001; #10;
        I = 4'b0010; #10;
        I = 4'b0111; #10;
        I = 4'b0100; #10;
        I = 4'b1010; #10;
        I = 4'b1111; #10;

    end
end
```

Multiplier code

Verilog code for 4-bit x2 multiplier

```
→ vvp q1.vvp
```

```
Solution by Adheesh Trivedi
```

```
=====
```

```
VCD info: dumpfile q1.vcd opened for output.
```

```
I      0      Carry
```

```
-----
```

```
0000 0000 0
```

```
0001 0010 0
```


```
0010 0100 0
```

```
0111 1110 0
```

```
0100 1000 0
```

```
1010 0100 1
```

```
1111 1110 1
```

 

Problem 2: 4-to-2 Encoder & 2-to-4 Decoder

Encoder and decoder implemented behaviorally.

```

module ENC4T02(
    input [3:0] I,
    output reg [1:0] O,
    output reg valid
);
    always @(I) begin
        case (I)
            4'b0001: begin O = 2'b00; valid = 1; end
            4'b0010: begin O = 2'b01; valid = 1; end
            4'b0100: begin O = 2'b10; valid = 1; end
            4'b1000: begin O = 2'b11; valid = 1; end
            default: begin O = 2'b00; valid = 0; end

            endcase
        end
    endmodule

`timescale 1ns / 1ps

module TEST();
    reg [3:0] I;
    wire [1:0] O;
    wire valid;

    ENC4T02 E(I, O, valid);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $display("I    O  Valid");
        $display("-----");
        $monitor("%b %b %b", I, O, valid);

        I = 4'b0000; #10;
        I = 4'b0001; #10;
        I = 4'b0010; #10;
        I = 4'b0011; #10;
        I = 4'b0100; #10;
        I = 4'b0101; #10;
        I = 4'b0110; #10;
        I = 4'b0111; #10;
        I = 4'b1000; #10;
        I = 4'b1111; #10;

    end

```

4-to-2 Encoder

```

module DEC2T04(
    input [1:0] I,
    output reg [3:0] O,
    output reg valid
);
    always @(I) begin
        case (I)
            2'b00: begin O = 4'b0001; valid = 1; end
            2'b01: begin O = 4'b0010; valid = 1; end
            2'b10: begin O = 4'b0100; valid = 1; end
            2'b11: begin O = 4'b1000; valid = 1; end
            default: begin O = 4'b0000; valid = 0; end

        endcase
    end
endmodule

`timescale 1ns / 1ps

module TEST();
    reg [1:0] I;
    wire [3:0] O;
    wire valid;

    DEC2T04 D(I, O, valid);

    initial begin
        $display("Solution by Adheesh Trivedi");
        $display("=====");
        $display("I  O    Valid");
        $display("-----");
        $monitor("%b %b %b", I, O, valid);

        I = 2'b00; #10;
        I = 2'b01; #10;
        I = 2'b10; #10;
        I = 2'b11; #10;

    end
endmodule

```

2-to-4 Decoder



→ vvp q2_enc.vvp

Solution by Adheesh Trivedi

=====

I 0 Valid

0000 00 0

0001 00 1

0010 01 1

0011 00 0

0100 10 1

0101 00 0

0110 00 0

0111 00 0

1000 11 1

1111 00 0



→ vvp q2_dec.vvp

Solution by Adheesh Trivedi

=====

I	0	Valid
---	---	-------

00	0001	1
----	------	---

01	0010	1
----	------	---

10	0100	1
----	------	---

11	1000	1
----	------	---

Problem 3: 8-to-1 Multiplexer

Case statement selects one of 8 inputs.

```
module MUX8T01(  
    input [7:0] I,  
    input [2:0] S,  
    output reg O  
);  
    always @(I, S) begin  
        case (S)  
            3'b000: O = I[0];  
            3'b001: O = I[1];  
            3'b010: O = I[2];  
            3'b011: O = I[3];  
            3'b100: O = I[4];  
            3'b101: O = I[5];  
            3'b110: O = I[6];  
            3'b111: O = I[7];  
            default: O = 1'b0;  
        endcase  
    end  
endmodule  
  
`timescale 1ns / 1ps  
  
module TEST();  
    reg [7:0] I;  
    reg [2:0] S;  
    wire O;  
endmodule
```

8-to-1 MUX



→ vvp q3.vvp

Solution by Adheesh Trivedi

=====

I S 0

000000000 000 0

000000001 000 1

000000010 001 1

000001000 010 1

000010000 011 1

000100000 100 1

001000000 101 1

010000000 110 1

100000000 111 1

111111111 111 1

101010101 101 1

010101010 010 1

Problem 4: 8-to-3 Priority Encoder

If-else logic encodes highest active input.

```
module PRIOENC8T03(  
    input [7:0] I,  
    output reg [2:0] O  
);  
    always @(I) begin  
        if (I[7]) begin O = 3'b111; end  
        else if (I[6]) begin O = 3'b110; end  
        else if (I[5]) begin O = 3'b101; end  
        else if (I[4]) begin O = 3'b100; end  
        else if (I[3]) begin O = 3'b011; end  
        else if (I[2]) begin O = 3'b010; end  
        else if (I[1]) begin O = 3'b001; end  
        else if (I[0]) begin O = 3'b000; end  
        else begin O = 3'b000; end  
    end  
endmodule  
  
`timescale 1ns / 1ps  
  
module TEST();  
    reg [7:0] I;  
    wire [2:0] O;  
  
    PRIOENC8T03 P(I, O);  
  
    initial begin  
        $display("Solution by Adheesh Trivedi");  
    end  
endmodule
```

8-to-3 Priority Encoder



→ vvp q4.vvp

Solution by Adheesh Trivedi

=====

I 0

00000000 000

00000001 000

00000010 001

00000100 010

00001000 011

00010000 100

00100000 101

01000000 110

10000000 111

11111111 111

10101010 111

01010101 110

Problem 5: 4-bit Carry Look-Ahead Adder

Adder uses carry look-ahead logic for fast sum.

```
module CARRY_LOOKAHEAD4 (  
    input [3:0] A,  
    input [3:0] B,  
    input Ci,  
    output reg [3:0] S,  
    output reg Co  
);  
    reg [3:0] P, G;  
    reg [3:0] C;  
    integer i;  
  
    always @(*) begin  
        G = A & B;  
        P = A ^ B;  
        C[0] = Ci;  
  
        // Ci+1 = Gi | Pi & Ci  
        for (i = 0; i < 3; i++) begin  
            C[i+1] = G[i] | (P[i] * C[i]);  
        end  
        Co = G[3] | (P[3] * C[3]);  
        S = P ^ C;  
  
    end  
endmodule  
  
`timescale 1ns / 1ps  
  
module TEST();  
    reg [3:0] A, B;  
    reg Ci;  
    wire [3:0] S;  
    wire Co;  
  
    CARRY_LOOKAHEAD4 CLA(A, B, Ci, S, Co);  
  
    initial begin  
        $display("Solution by Adheesh Trivedi");  
    end  
endmodule
```

Carry Look-Ahead Adder



→ vvp q5.vvp

Solution by Adheesh Trivedi

=====

A	B	Ci		S	Co
---	---	----	--	---	----

0000	0000	0		0000	0
0001	0001	0		0010	0
0010	0011	0		0101	0
0100	0101	0		1001	0
1010	1001	0		0011	1
1111	1111	0		1110	1
0000	0000	1		0001	0
0001	0001	1		0011	0
0010	0011	1		0110	0
0100	0101	1		1010	0
1010	1001	1		0100	1
1111	1111	1		1111	1

Problem 6: 4-bit Wallace Tree Multiplier

Wallace tree structure for fast multiplication.

```

module HALF_ADDER (
    input A,
    input B,
    output S,
    output C
);
    assign S = A ^ B;
    assign C = A & B;

endmodule

module FULL_ADDER (
    input A,
    input B,
    input Ci,
    output S,
    output Co
);
    assign S = A ^ B ^ Ci;
    assign Co = A & B | ((A | B) & Ci);

endmodule

module WALLACE_TREE_MULT4 (
    input [3:0] A,
    input [3:0] B,
    output [7:0] M
);
    // Partial products
    wire [3:0] P0, P1, P2, P3;

    // Generate partial products
    assign P0 = A & {4{B[0]}};
    assign P1 = A & {4{B[1]}};
    assign P2 = A & {4{B[2]}};
    assign P3 = A & {4{B[3]}};

    // Intermediate wires for carries and sums
    wire c1, c2, c3, c4, c5, c6, c7, c8, c9, c10, c11; // added c11
    wire s1, s2, s3, s4, s5, s6; // removed unused s7,s8,s9

    // First bit (no addition needed)
    assign M[0] = P0[0];

    // Second bit
    HALF_ADDER ha1 (P0[1], P1[0], M[1], c1);

```

Wallace Tree Multiplier



→ vvp q6.vvp

Solution by Adheesh Trivedi

=====

A	B		M

0	0		0
4	5		20
10	9		90
15	15		225
1	1		1
2	3		6
6	3		18
9	14		126