

ECS 409: Computer Organization – Assignment 3

Adheesh Trivedi

2025-09-13

Problem 1: SR Latch with Enable & Reset

Simple SR latch with async enable and reset; holds state when En=0, reset dominates.

```
`timescale 1ns / 1ps

module SR_LATCH (
    input S, R, En, Rst,
    output reg Q
);
    always @(*) begin
        // Asynchronous Reset dominates
        if (Rst) Q = 0;
        else if (En) begin
            if (S & ~R) begin
                Q = 1;
            end else if (~S & R) begin
                Q = 0;
            end
        end
    end
endmodule

module TEST();
    reg S, R, En, Rst;
    wire Q;

    SR_LATCH uut (S, R, En, Rst, Q);

    initial begin
        $dumpfile("q1.vcd");
        $dumpvars(0, TEST);
        $display("Solution by Adheesh Trivedi");
        $display("=====");

        $display("");
        $display("S R En Rst Q");
        $display("-----");
        $monitor("%b %b %b %b %b", S, R, En, Rst, Q);

        // Asynchronous Reset
        S = 0; R = 0; En = 0; Rst = 1; #5;
        Rst = 0; #5;
        // Set
        S = 1; R = 0; En = 1; #5;
        S = 0; #5;
        // Reset
        S = 0; R = 1; En = 1; #5;
        R = 0; En = 0; #5;
        // Not Enabled
        S = 1; R = 0; #5;
        // Enabled again
        En = 1; #5;
        S = 0; #10;
    end
endmodule
```

```
end
endmodule
```


SR latch with En & Rst

1.1 Simulation Output

Q resets when Rst=1 regardless of inputs; when enabled, S=1 sets and R=1 resets. Transitions match table in outputs (stable hold when En=0; no illegal set when R=1).

```
→ vvp q1.vvp
VCD info: dumpfile q1.vcd opened for output.
Solution by Adheesh Trivedi
=====
```

S	R	En	Rst	Q
0	0	0	1	0
0	0	0	0	0
1	0	1	0	1
0	0	1	0	1
0	1	1	0	0
0	0	0	0	0
1	0	0	0	0
1	0	1	0	1
0	0	1	0	1

 

Problem 2: Improved D Latch with Gate Delays

Behavioral D latch with 1 ns gate delays; shows correct level-sensitive behavior.

```
`timescale 1ns / 1ps

module d_latch (
    input D, CLK,
    output reg Q
);
    reg N1, N2, not_CLK;

    initial Q = 0;

    always @(D or CLK or not_CLK or N1 or N2 or Q) begin
        #1 N1 = D & CLK;
        #1 not_CLK = ~CLK;
        #1 N2 = not_CLK & Q;
        #1 Q = N1 | N2;
    end

endmodule

module TEST();
    reg D, CLK;
    wire Q;

    d_latch dl (D, CLK, Q);

    initial CLK = 0;
    always begin
        #10; CLK = ~CLK;
    end

    initial begin
        $dumpfile("q2.vcd");
        $dumpvars(0, TEST);
        $display("Solution by Adheesh Trivedi");
        $display("=====");

        $display("");
        $display("Time  D CLK Q");
        $display("-----");
        $monitor("%5t %b %b %b", $time, D, CLK, Q);

        D = 0; #9;
        D = 1; #13;
        D = 0; #16;
        D = 1; #21;
        D = 0; #26;

        $finish;
    end
endmodule
```

Improved D latch (1ns delays)

2.1 Simulation Output


Q follows D only while CLK=1 after 1 ns delay; holds value when CLK=0. Edges and printed times (e.g., 10k, 30k ps) match expected delayed response.

```

→ vvp q2.vvp
VCD info: dumpfile q2.vcd opened for output.
Solution by Adheesh Trivedi
=====

Time   D CLK Q
-----
      0 0  0  0
    9000 1  0  0
   10000 1  1  0
   13000 1  1  1
   20000 1  0  1
   22000 0  0  1
   30000 0  1  1
   34000 0  1  0
   38000 1  1  0
   40000 1  0  0
   42000 1  0  1
   50000 1  1  1
   59000 0  1  1
   60000 0  0  1
   70000 0  1  1
   74000 0  1  0
   80000 0  0  0
q2.v:49: $finish called at 85000 (1ps)

```

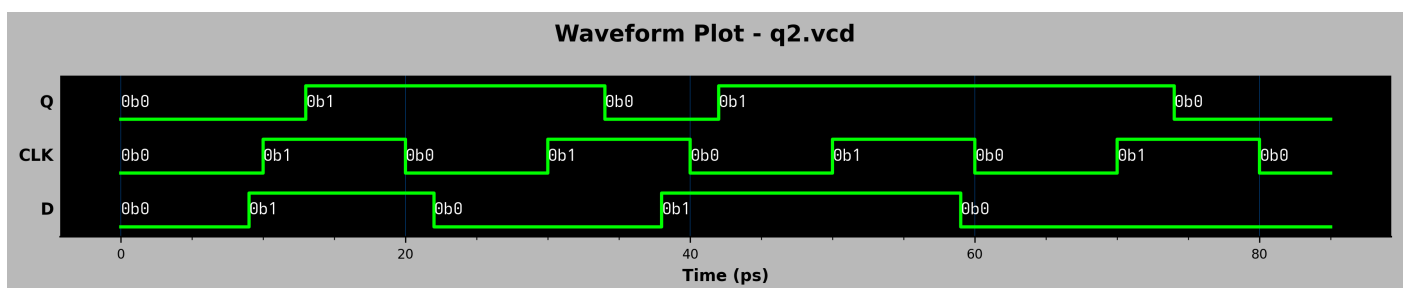

Problem 3: 3-bit Down Counter (7 to 0)

Counts 7→0 and repeats; synchronous reset initializes to 000.

```
`timescale 1ns / 1ps

module COUNTER(
    input wire CLK, Rst,
    output reg [2:0] Q
);
    initial Q = 3'b000;

    always @(posedge CLK or posedge Rst) begin
        // Prioritize reset
        if (Rst) begin
            Q <= 3'b000;
        end else begin
            Q <= Q - 1;
        end
    end
endmodule

module TEST();
    reg CLK, Rst;
    wire [2:0] Q;

    COUNTER uut (CLK, Rst, Q);

    always begin
        #5;
        CLK = ~CLK;
    end

    initial begin
        $dumpfile("q3.vcd");
        $dumpvars(0, TEST);
        $display("Solution by Adheesh Trivedi");
        $display("=====");

        $display("");
        $display("Rst  Q");
        $display("-----");
        $monitor("%2b  %b", Rst, Q);

        CLK = 0; Rst = 1; #10;
        Rst = 0;
        #57;


        Rst = 1; #10;
        Rst = 0; #80;

        $finish;
    end
endmodule
```

Mod-8 down counter

3.1 Simulation Output

Sequence shows 111→110→...→000 then wrap; Rst forces 000 then counts down again. Printed log confirms two full cycles and final wrap as in outputs.txt.

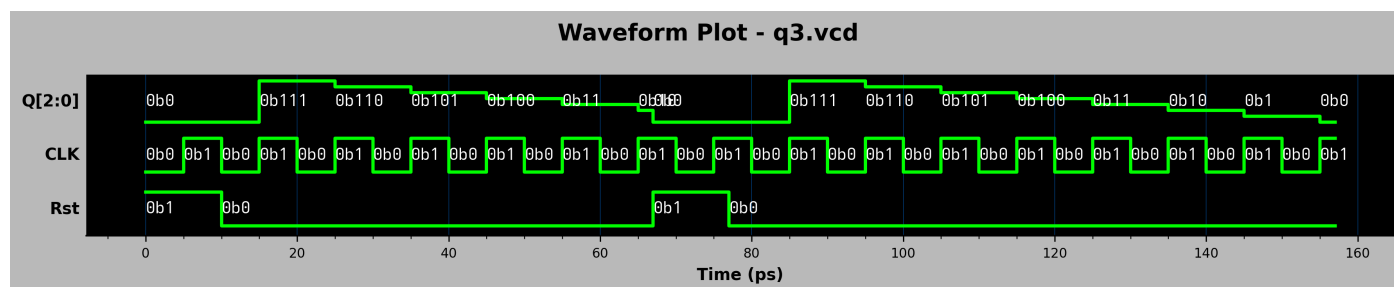

Problem 4: Mod-8 Gray Code Counter with UP

Gray code transitions change one bit per step; UP selects advance or hold.

```
`timescale 1ns / 1ps

module GRAY_COUNTER (
    input CLK, input Rst, input UP,
    output reg [2:0] Q
);
    initial Q = 3'b000;

    always @(posedge CLK or posedge Rst) begin
        if (Rst) begin
            Q <= 3'b000;
            // Derived from K-MAPS
        end else if (UP) begin
            Q[0] <= ~ (Q[1] ^ Q[2]);
            Q[1] <= Q[0] ? ~Q[2] : Q[1];
            Q[2] <= Q[0] ? Q[2] : Q[1];
        end
    end
endmodule

module TEST();
    reg CLK, Rst, UP;
    wire [2:0] Q;

    GRAY_COUNTER gc (CLK, Rst, UP, Q);

    initial CLK = 0;

    always begin
        #5; CLK = ~CLK;
    end

    initial begin
        $dumpfile("q4.vcd");
        $dumpvars(0, TEST);
        $display("Solution by Adheesh Trivedi");
        $display("=====");

        $display("");
        $display("UP Q");
        $display("-----");
        $monitor("%b %b", UP, Q);

        Rst = 1; UP = 1; #6;
        Rst = 0; #44;
        UP = 0; #8;
        UP = 1; #42;

        $finish;
    end
endmodule
```

UP/DOWN Gray code counter

4.1 Simulation Output


Logs show single-bit changes and holds when UP=0; wrap-around behavior verified. Waveform matches printed sequence (e.g., 000→001→011→010→110...).

```

→ vvp q4.vvp
VCD info: dumpfile q4.vcd opened for output.
Solution by Adheesh Trivedi
=====

UP Q
-----
1 000
1 001
1 011
1 010
1 110
0 110
1 110
1 111
1 101
1 100
1 000
q4.v:50: $finish called at 100000 (1ps)

```

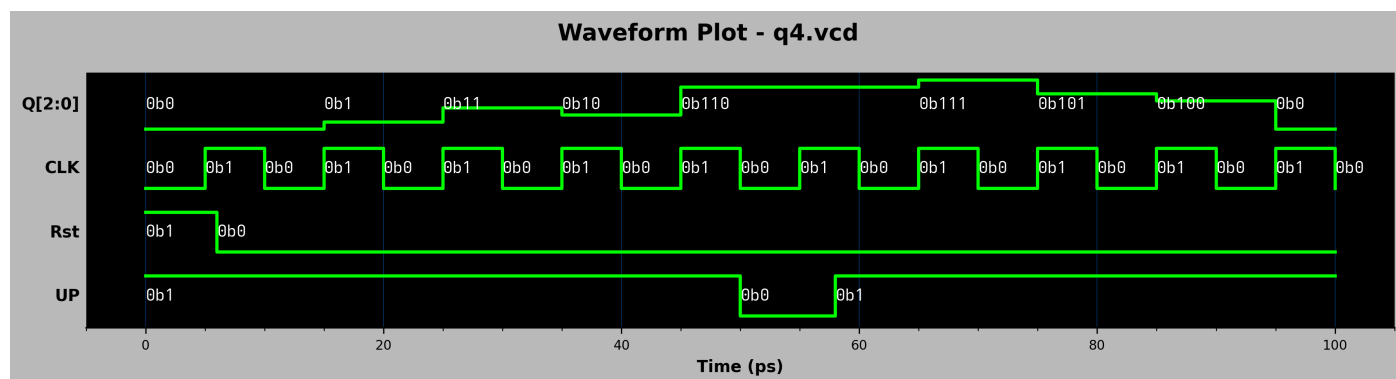

Problem 5: Parameterized N-bit Bidirectional Shift Register

Shift left/right under DIR with enable; parameter N configures width.

```
`timescale 1ns / 1ps

module N_BIT_BIDIR_SHIFT_REG #(parameter MSB = 8) (
    input wire D, CLK, En, DIR, Rstn,
    output reg [MSB-1:0] OUT
);
    initial OUT = {MSB{1'b0}};

    always @(posedge CLK) begin
        if (!Rstn) begin
            OUT <= {MSB{1'b0}};
        end else if (En) begin
            case (DIR)
                1'b0: OUT <= {OUT[MSB-2:0], D};
                1'b1: OUT <= {D, OUT[MSB-1:1]};
            endcase
        end
    end
endmodule

module TEST();

    reg D, CLK, En, DIR, Rstn;
    wire [7:0] OUT;

    N_BIT_BIDIR_SHIFT_REG #(8) nbbsr (
        D, CLK, En, DIR, Rstn, OUT
    );

    initial CLK = 0;
    always begin
        #5; CLK = ~CLK;
    end

    initial begin
        $dumpfile("q5.vcd");
        $dumpvars(0, TEST);
        $display("Solution by Adheesh Trivedi");
        $display("=====");

        $display("");
        $display("Time    CLK Rstn En DIR D    OUT");
        $display("-----");
        $monitor("%6t %b    %b    %b    %b    %b    %b", $time, CLK, Rstn, En, DIR, D, OUT);

        // Reset low for a couple of clock edges (synchronous reset)
        D = 0; En = 0; DIR = 0; Rstn = 0; #12;
        Rstn = 1; #8;

        // Enable and shift left (DIR=0) while feeding data bits
        En = 1; DIR = 0;
        D = 1; #10;
        D = 0; #10;
        D = 1; #10;
        D = 1; #10;
    end
endmodule
```

Parametric bidirectional shifter

Output shifts as DIR changes and En toggles; patterns match table in log. Reset deassert then enable drives series of shifts, mirroring outputs.txt.



```

→ vvp q5.vvp
VCD info: dumpfile q5.vcd opened for output.
Solution by Adheesh Trivedi
=====

Time    CLK Rstn En DIR D    OUT
-----
    0 0      0  0  0  0    00000000
 5000 1      0  0  0  0    00000000
10000 0      0  0  0  0    00000000
12000 0      1  0  0  0    00000000
15000 1      1  0  0  0    00000000
20000 0      1  1  0  1    00000000
25000 1      1  1  0  1    00000001
30000 0      1  1  0  0    00000001
35000 1      1  1  0  0    00000010
40000 0      1  1  0  1    00000010
45000 1      1  1  0  1    00000101
50000 0      1  1  0  1    00000101
55000 1      1  1  0  1    00001011
60000 0      1  1  1  0    00001011
65000 1      1  1  1  0    00000101
70000 0      1  1  1  1    00000101
75000 1      1  1  1  1    10000010
80000 0      1  1  1  0    10000010
85000 1      1  1  1  0    01000001
90000 0      1  0  0  1    01000001
95000 1      1  0  0  1    01000001
100000 0      1  0  0  1    01000001
105000 1      1  0  0  1    01000001
110000 0      1  1  0  1    01000001
115000 1      1  1  0  1    10000011
120000 0      1  1  0  1    10000011
125000 1      1  1  0  1    00000111
130000 0      1  1  0  1    00000111
135000 1      1  1  0  1    00001111
140000 0      1  1  0  1    00001111
q5.v:70: $finish called at 142000 (1ps)

```

Problem 6: 128×16 Single-Port Memory

Synchronous write on WE; combinational read returns stored data.

```
`timescale 1ns / 1ps

module MEMORY_1P (
    input wire clk, we,
    // address
    input wire [6:0] waddr, raddr,
    // Data input
    input wire [15:0] Din,
    // Data output
    output reg [15:0] rdata, wdata
);
    reg [15:0] mem [0:127];

    integer i;
    initial begin
        // Initialize memory to 0 for determinism
        for (i = 0; i < 128; i = i + 1) begin
            mem[i] = 16'h0000;
        end
        rdata = 16'h0000;
        wdata = 16'h0000;
    end

    always @(posedge clk) begin
        // Write path
        if (we) begin
            mem[waddr] <= Din;
            wdata <= Din;
        end

        // Read path: write-first if raddr == waddr and we is asserted
        if (we && (waddr == raddr)) begin
            rdata <= Din;
        end else begin
            rdata <= mem[raddr];
        end
    end
endmodule

module TEST();
    reg clk, we;
    reg [6:0] waddr, raddr;
    reg [15:0] Din;
    wire [15:0] rdata, wdata;

    MEMORY_1P mem (
        clk, we, waddr, raddr, Din, rdata, wdata
    );

    initial clk = 0;
    always begin
        #5; clk = ~clk;
    end

    initial begin
        $dumpfile("q6.vcd");
    end
endmodule
```

```

$dumpvars(0, TEST);
$display("Solution by Adheesh Trivedi");
$display("=====");

$display("");
$display("Time   clk we waddr raddr   Din   | rdata   wdata");
$display("-----");
$monitor("%6t %b   %b %3d   %3d   0x%04h | 0x%04h   0x%04h", $time, clk, we, waddr, raddr,
Din, rdata, wdata);

// Initial
we = 0; waddr = 0; raddr = 0; Din = 16'h0000; #12;

// Write some locations
we = 1; waddr = 7'd3;   Din = 16'hABCD; raddr = 7'd0; #10;
we = 1; waddr = 7'd5;   Din = 16'h1234; raddr = 7'd3; #10;
we = 1; waddr = 7'd127; Din = 16'hDEAD; raddr = 7'd5; #10;

// Read back
we = 0; raddr = 7'd3; #10;
raddr = 7'd5; #10;
raddr = 7'd127; #10;

// Same-cycle write/read to same address -> write-first behavior
we = 1; waddr = 7'd8; raddr = 7'd8; Din = 16'hBEEF; #10;
we = 0; raddr = 7'd8; #10;

// Hold read while writing elsewhere
raddr = 7'd5; we = 1; waddr = 7'd9; Din = 16'hCAFE; #10;
we = 0; #10;


$finish;
end
endmodule

```

Single-port RAM 128×16

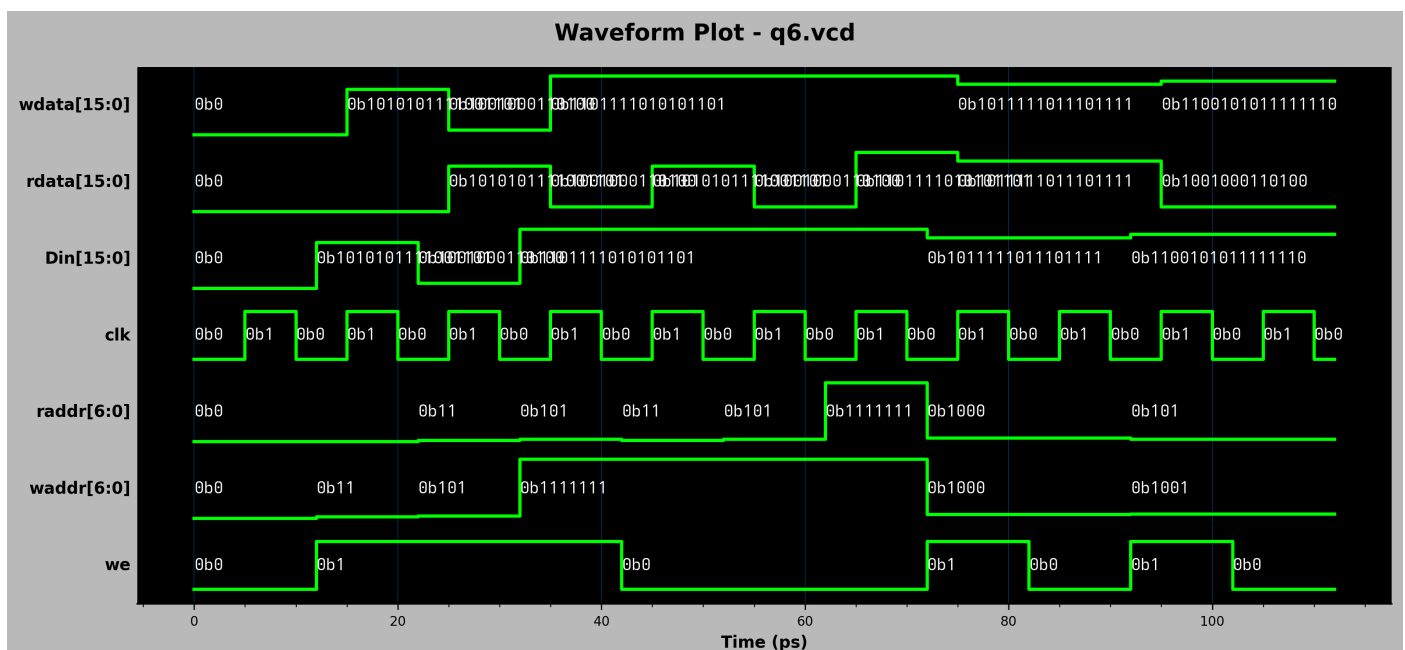6.1 Simulation Output

Writes at addresses 3,5,127,8,9 then reads back matching data (abcd,1234,dead,beef,cafe). Printed time-stamped table confirms correct read-after-write and later reads.



→ vvp q6.vvp

VCD info: dumpfile q6.vcd opened for output.

Solution by Adheesh Trivedi

=====

Time	clk	we	waddr	raddr	Din	rdata	wdata
0	0	0	0	0	0x0000	0x0000	0x0000
5000	1	0	0	0	0x0000	0x0000	0x0000
10000	0	0	0	0	0x0000	0x0000	0x0000
12000	0	1	3	0	0xabcd	0x0000	0x0000
15000	1	1	3	0	0xabcd	0x0000	0xabcd
20000	0	1	3	0	0xabcd	0x0000	0xabcd
22000	0	1	5	3	0x1234	0x0000	0xabcd
25000	1	1	5	3	0x1234	0xabcd	0x1234
30000	0	1	5	3	0x1234	0xabcd	0x1234
32000	0	1	127	5	0xdead	0xabcd	0x1234
35000	1	1	127	5	0xdead	0x1234	0xdead
40000	0	1	127	5	0xdead	0x1234	0xdead
42000	0	0	127	3	0xdead	0x1234	0xdead
45000	1	0	127	3	0xdead	0xabcd	0xdead
50000	0	0	127	3	0xdead	0xabcd	0xdead
52000	0	0	127	5	0xdead	0xabcd	0xdead
55000	1	0	127	5	0xdead	0x1234	0xdead
60000	0	0	127	5	0xdead	0x1234	0xdead
62000	0	0	127	127	0xdead	0x1234	0xdead
65000	1	0	127	127	0xdead	0xdead	0xdead
70000	0	0	127	127	0xdead	0xdead	0xdead
72000	0	1	8	8	0xbeef	0xdead	0xdead
75000	1	1	8	8	0xbeef	0xbeef	0xbeef
80000	0	1	8	8	0xbeef	0xbeef	0xbeef
82000	0	0	8	8	0xbeef	0xbeef	0xbeef
85000	1	0	8	8	0xbeef	0xbeef	0xbeef
90000	0	0	8	8	0xbeef	0xbeef	0xbeef
92000	0	1	9	5	0xcafe	0xbeef	0xbeef
95000	1	1	9	5	0xcafe	0x1234	0xcafe
100000	0	1	9	5	0xcafe	0x1234	0xcafe
102000	0	0	9	5	0xcafe	0x1234	0xcafe
105000	1	0	9	5	0xcafe	0x1234	0xcafe
110000	0	0	9	5	0xcafe	0x1234	0xcafe

q6.v:88: \$finish called at 112000 (1ps)